

# CS 250: Computer Architecture

## Final Exam

### Spring 2025

Benjamin Lobos Lertpunyaroj

*May 8th, 10:30<sub>AM</sub> – 12:30<sub>PM</sub>*

#### Exam contents and details for referencing

- Final exam is held in Fowler Hall on May 8th (Thursday), from 10:30 <sub>AM</sub> to 12:30 <sub>PM</sub>.
- Previous cumulative book chapters
  - Chapter 1 sections 1, 2, and 3.
  - Chapter 2, sections 1, 2, 3, 4, 5, 6, and 7.
  - Chapter 3, sections 1, 2, and 5.
  - Chapter 4, sections 1, 2, 3, 4, 5, 6, 7, and 8.
  - Chapter 5, sections 1, 2, 3, 4, 7, and 8.
  - Chapter 8 (Appendix A), sections 1, 2, 3 (but not PLAs or ROMs), 5, 7 (lightly), and 8.
- All lecture notes and lecture slides.
- All labs (1 - 11).

# Appendix A

## Logic & Gates

An *asserted* signal is logically true, the *deasserted* is the opposite.

### Two types of logic systems

**Combinational logic:** No memory in components, hence same output given same input.

**Sequential logic:** Memory in components, hence output depends on input and current memory state.

 


Figure 1: AND gate, OR gate, and inverter

The gates can be combined to form different forms of logic. An example of this is  $\overline{\overline{A} + \overline{B}}$  which is equivalent to  $A \cdot B$  by De Morgan's law, seen in Figure 2.

 


Figure 2: Logic gate implementation of example formula

## Decoders & Multiplexors

A **decoder** is a logic block that has an  $n$ -bit input and  $2^n$  outputs, where there is one unique true bit as output from a unique set of bytes of input.

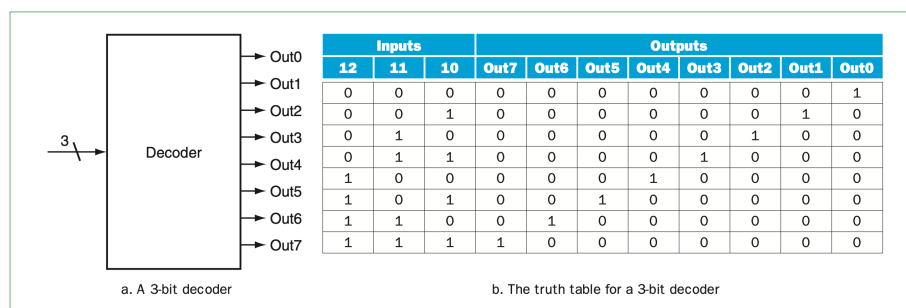


Figure 3: 3-bit input decoder that generates  $2^3 = 8$  different outputs (Out0 – Out7)

$$2^n \text{ outputs} \therefore \log_2(\text{output}) = \text{input bits}$$

Encoders are the other way around.

**Multiplexors** have a selector input (or control value), that will determine which inputs will become outputs.

In the case of the two-input MUX, its representation is the following,  $C = (A \cdot \bar{S}) + (B \cdot S)$ , using  $n$  (data inputs) AND gates, and one OR gate.

 


Figure 4: Two-input multiplexor that generates one output depending on the selector input  $S$

$$n \text{ (data inputs)} \therefore \log_2 n = S \text{ selector bits required to represent all inputs}$$

Often times a decoder generates  $n$  bits for a MUX, to be used as a selector signal.

## Buses

A collection of data lines that is treated as a single logical signal.

When showing a logic unit whose inputs and outputs are buses, the unit must be replicated a sufficient number of times to accommodate the width of the input.

You can use multiplexors to select between two buses, requiring  $n$  inputs to represent  $n$ -bit buses.

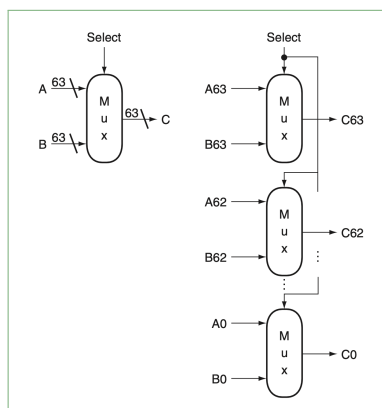


Figure 5: 1-bit multiplexors replicated 64 times to represent two 64-bit buses

## ALUs

### Operation done by the ALU

**Logic operations:** AND and OR gate operations, with NOR being available through an inversion of both input signals with AInvert and BInvert control signals.

**Arithmetic operations:** Addition and subtraction through the full adder, and BInvert control signal on one input for determining the type of operation.

The LEGv8 word is 64 bits wide, as such a 64 bit wide ALU is required (64 1-bit ALUs).

In its simplest form, a 1-bit logical unit for AND and OR operations simply requires a multiplexor and a one bit control signal to select between the two operations ( $2^1 = 2$ ).

 


Figure 6: 1-bit logical unit for AND and OR operations

Implementing addition requires two input operands, one output, a CarryIn bit carried from the less-significant bits of the operation (i.e. another 1-bit logical unit), and a CarryOut bit to be carried forward to the next more significant bit.

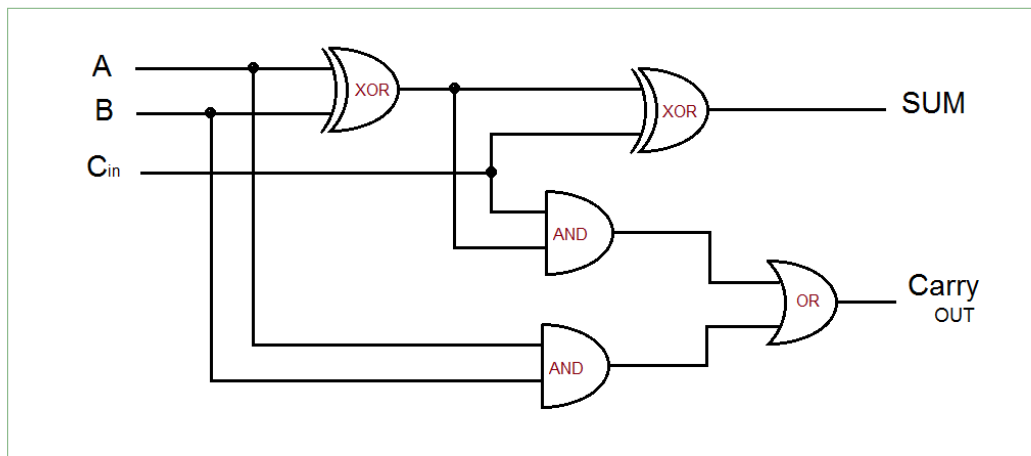


Figure 7: Full adder that performs mod 2 addition

The combination of the adder and the logic gates, coupled with a multiplexor with a control signal to determine the operation makes a complete 1-bit ALU, which can be seen in Figure 8.

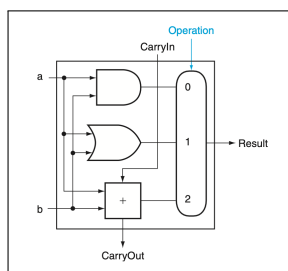


Figure 8: 1-bit alu with logical operations and addition

For expanding to a 64-bit ALU, the adders have to set up a ripple carry from the least to the most significant bit.

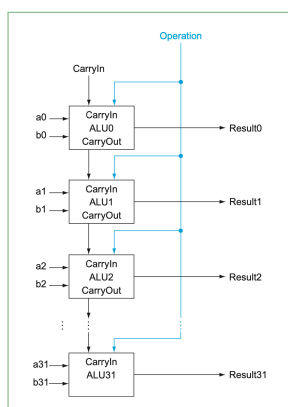


Figure 9: Ripple carry implemented for a 64-bit ALU

By inverting the second input (**BInvert** = 1, seen in Figure 10) and setting **CarryIn** to 1 in the least significant bit of the ALU, we get two's complement subtraction of **b** from **a**.

To implement a NOR function, existing components can be combined,  $\overline{(a + b)} = \bar{a} \cdot \bar{b}$  (DeMorgan's theorem), which means we need an AND and two inverters for both **a** and **b**, seen in Figure 10

 


Figure 10: 1-bit ALU that performs subtraction, and NOR operations

On a 64-bit ALU we can use a zero flag to help with conditional branch instructions in LEGv8 (e.g.

CBZ), as they receive to inputs and require to test if the subtraction has a zero.

The following represents this with an inversion of an OR tree on all results from the subtraction considering a 64-bit subtraction, fully represented in Figure 11.

$$Zero = \overline{(R_0 + R_1 + R_2 + \dots + R_{63})}$$

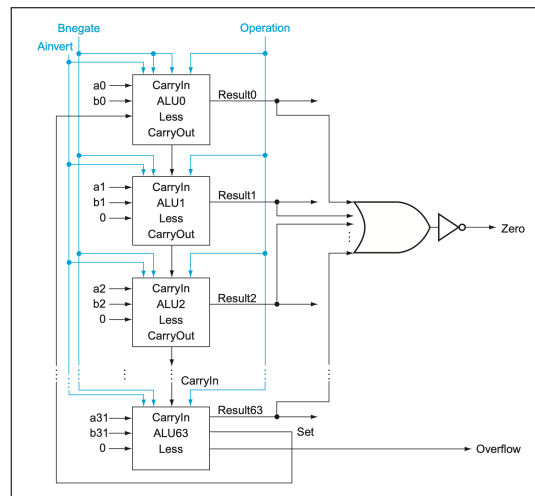


Figure 11: 64-bit ALU OR tree and an inverter for determining the Zero flag

For a generalized symbol of the ALU, Figure 12, where ALU operation is the control signal of the MUX that determines the type of operation.

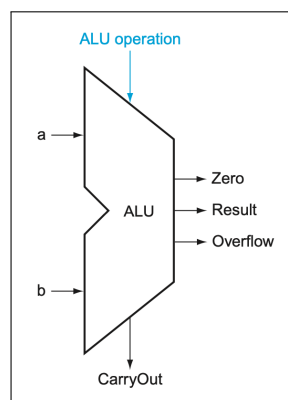


Figure 12: General symbol for an ALU or an adder

## Clocks