

# CS 250: Computer Architecture

## Final Exam

### Spring 2025

Benjamin Lobos Lertpunyaroj

*May 8th, 10:30<sub>AM</sub> – 12:30<sub>PM</sub>*

#### Exam contents and details for referencing

- Final exam is held in Fowler Hall on May 8th (Thursday), from 10:30 <sub>AM</sub> to 12:30 <sub>PM</sub>.
- Previous cumulative book chapters
  - Chapter 1 sections 1, 2, and 3.
  - Chapter 2, sections 1, 2, 3, 4, 5, 6, and 7.
  - Chapter 3, sections 1, 2, and 5.
  - Chapter 4, sections 1, 2, 3, 4, 5, 6, 7, and 8.
  - Chapter 5, sections 1, 2, 3, 4, 7, and 8.
  - Chapter 8 (Appendix A), sections 1, 2, 3 (but not PLAs or ROMs), 5, 7 (lightly), and 8.
- All lecture notes and lecture slides.
- All labs (1 - 11).

# Appendix A

## Logic & Gates

An *asserted* signal is logically true, the *deasserted* is the opposite.

### Two types of logic systems

**Combinational logic:** No memory in components, hence same output given same input.

**Sequential logic:** Memory in components, hence output depends on input and current memory state.

 


Figure 1: *AND gate, OR gate, and inverter*

The gates can be combined to form different forms of logic. An example of this is  $\overline{\overline{A} + B}$  which is equivalent to  $A \cdot \overline{B}$  by De Morgan's law, seen in Figure 2.

 


Figure 2: *Logic gate implementation of example formula*

## Decoders & Multiplexors

A **decoder** is a logic block that has an  $n$ -bit input and  $2^n$  outputs, where there is one unique true bit as output from a unique set of bytes of input.

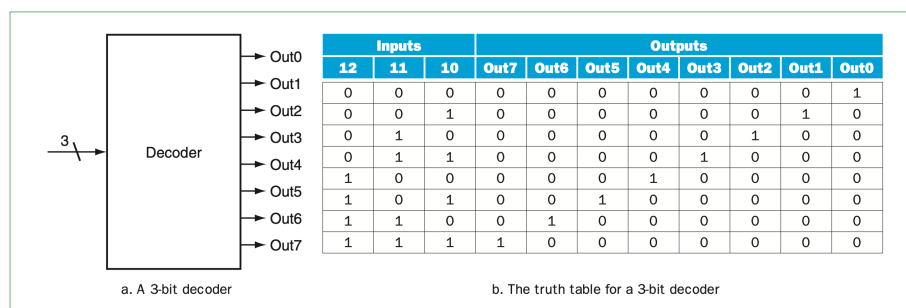


Figure 3: *3-bit input decoder that generates  $2^3 = 8$  different outputs (Out0 – Out7)*

$$2^n \text{ outputs } \therefore \log_2(\text{output}) = \text{input bits}$$

Encoders are the other way around.

**Multiplexors** have a selector input (or control value), that will determine which inputs will become outputs.

In the case of the two-input MUX, its representation is the following,  $C = (A \cdot \bar{S}) + (B \cdot S)$ , using  $n$  (data inputs) AND gates, and one OR gate.

 


Figure 4: *Two-input multiplexor that generates one output depending on the selector input  $S$*

$$n \text{ (data inputs)} \therefore \log_2 n = S \text{ selector bits required to represent all inputs}$$

Often times a decoder generates  $n$  bits for a MUX, to be used as a selector signal.